

Tutorial 02

(01) Imagine you have two inputs A and B, and you want to design a logical circuit that outputs A 1 if and only if


- A is a 0, and B is a 1
- or
- A is a 1, and B is a 0

Which logic gate would you use to create this circuit.

A	B	output
0	0	0
0	1	1
1	0	1
1	1	0

XOR gate

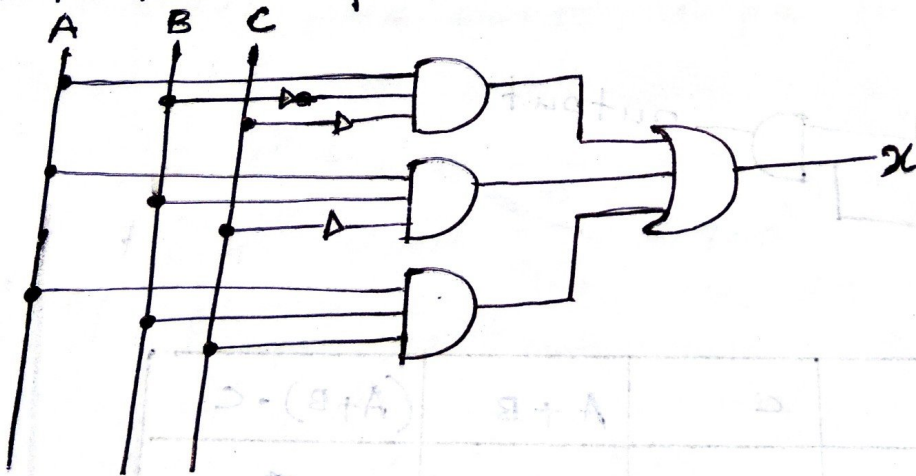(02) Consider the logic circuit shows the figure in which A, B and C are the inputs and X is the output.



Draw the logical circuit.

$$X = (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot B \cdot \bar{C}) + (A \cdot B \cdot C)$$

A	B	C	\bar{B}	\bar{C}	$A \cdot \bar{B} \cdot \bar{C}$	$A \cdot B \cdot \bar{C}$	$A \cdot B \cdot C$	X
0	0	0	1	1	0	0	0	0
0	0	1	1	0	0	0	0	0
0	1	0	0	1	0	0	0	0
0	1	1	0	0	0	0	0	0
1	0	0	1	1	1	0	0	1
1	0	1	1	0	0	0	0	0
1	1	0	0	1	0	1	0	1
1	1	1	0	0	0	0	1	1

(Q3) Condition

The output x of a logic circuit that devices the display of the alert must have a value of 1 when either one of the conditions is met.

• Carbon dioxide pressure too low and temperature $> 300^{\circ}\text{C}$ ~~AND~~ OR

• Water pressure $> 10 \text{ pa}$ and temp $> 300^{\circ}\text{C}$

Carbon dioxide pressure — A $\begin{matrix} \swarrow 1 \text{ low} \\ \searrow 0 \end{matrix}$ high

temperature B $\begin{matrix} \swarrow 1 > 300^{\circ}\text{C} \\ \searrow 0 < 300^{\circ}\text{C} \end{matrix}$

Water pressure C $\begin{matrix} \swarrow 1 > 10 \text{ pa} \\ \searrow 0 < 10 \text{ pa} \end{matrix}$

A	B	C	$A \cdot B$	$C \cdot B$	$(A \cdot B) + (C \cdot B)$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	1	1
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	1	0	1
1	1	1	1	1	1